

## WISH - 2026 - Inductors

\* Full Name


V

\* WISH Participant ID

wish26007

Q1. For the below circuit, the initial current through the inductor is 0A. Find  $V_x$  and  $V_y$  at time  $t=5s$ ?

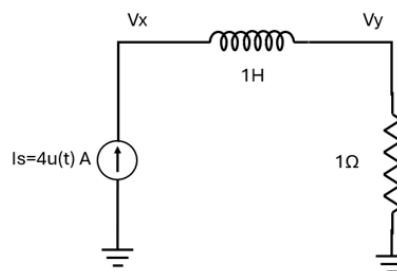- (a)  $V_x=0V$ ;  $V_y=0V$
- (b)  $V_x=4V$ ;  $V_y=0V$
- (c)  $V_x=0V$ ;  $V_y=4V$
- (d)  $V_x=4V$ ;  $V_y=4V$
- (e)  $V_x=\infty V$ ;  $V_y=0V$
- (f)  $V_x=0V$ ;  $V_y=\infty V$
- (g)  $V_x=\infty V$ ;  $V_y=\infty V$
- (h)  $V_x=0V$ ;  $V_y=1V$



Answer the Question 1

☐ a

☐ e

☐ b

☐ f

☐ c


☐ g

☐ d

☐ h

Q2. For the below circuit  $V_s(t)=2u(t)+4u(t-1)$  and  $I_L(t=0^-)=0A$ . What is the current through the inductor at  $t=5s$ ?

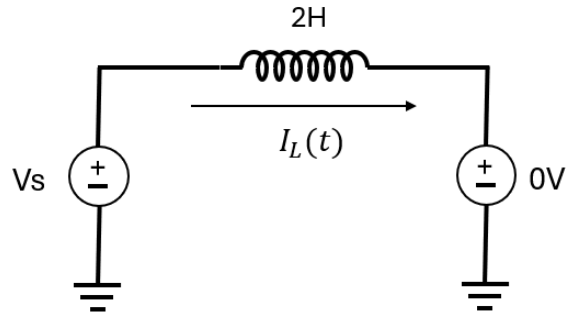- (a) 9A
- (b) 10A
- (c) 11A
- (d) 12A
- (e) 13A
- (f) 14A
- (g) 15A
- (h) 16A



Answer the Question 2

☐ a

☐ e

☐ b

☐ f

☐ c


☐ g

☐ d

☐ h

Q 3. For the below circuit  $V_s(t)=2u(t)$  V,  $I_s(t)=2r(t)$  A, and  $I_L(t=0^-)=0A$ . What is the voltage at X at 1s?

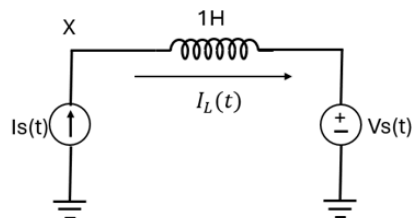- (a) 0 V
- (b) 1 V
- (c) 2 V
- (d) 3 V
- (e) 4 V
- (f) 5 V
- (g) 6 V
- (h) 7 V



Answer the Question 3

☐ a

☐ e

☐ b

☐ f

☐ c

☐ g

☐ d

☐ h

Q 4. For the below circuit the initial currents through the inductors are 0A. S1 is closed at  $t=0$ s. Find  $I_1$  at  $t=0^+$  and  $t=\infty$ ?

(a)  $I_1(t=0^+) = \frac{3}{4}A$ ;  $I_1(\infty) = 1A$

(b)  $I_1(t=0^+) = \frac{1}{4}A$ ;  $I_1(\infty) = 0A$

(c)  $I_1(t=0^+) = 1A$ ;  $I_1(\infty) = 1A$


(d)  $I_1(t=0^+) = 0A$ ;  $I_1(\infty) = 0A$

(e)  $I_1(t=0^+) = \frac{1}{2}A$ ;  $I_1(\infty) = \frac{1}{2}A$

(f)  $I_1(t=0^+) = \infty A$ ;  $I_1(\infty) = 0A$

(g)  $I_1(t=0^+) = 0A$ ;  $I_1(\infty) = \infty A$

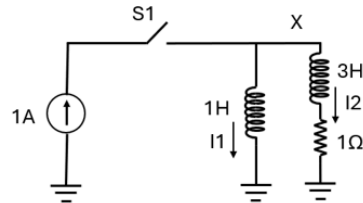(h)  $I_1(t=0^+) = \infty A$ ;  $I_1(\infty) = \infty A$



Answer the Question 4

☐ a

☐ e

☐ b

☐ f

☐ c

☐ g

☐ d

☐ h

Q5. In question 4, the highest instantaneous voltage at node X is

(a) 0V

(b)  $\infty V$

(c) 1V

(d) 10V

(e)  $-\infty V$

(f) -1V

(g) -10V

(h) -4V

Answer the Question 5

☐ a

☐ e

☐ b

☐ f

☐ c


☐ g

☐ d

☐ h

Q6. The circuit below has switch S1 in closed state for a very long time. At  $t=0$ , S1 is suddenly opened. What is the voltage at node VL at  $t = 0^+$ ?

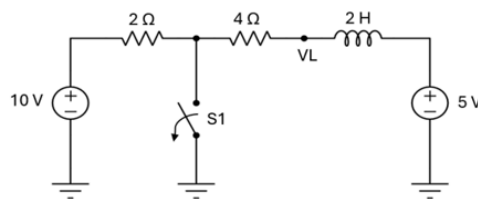- (a) -12.5 V
- (b) -5 V
- (c) -3.33 V
- (d) 0
- (e) 2.5 V
- (f) 6.66 V
- (g) 10 V
- (h) 17.5 V



Answer the Question 6

☐ a

☐ e

☐ b

☐ f

☐ c


☐ g

☐ d

☐ h

Q7. What is the value of R in the circuit below such that energies stored in the inductor and capacitor are equal at  $t = \infty$ ?

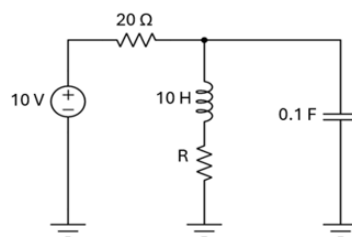- (a) 1  $\Omega$
- (b) 2.5  $\Omega$
- (c) 4  $\Omega$
- (d) 8.66  $\Omega$
- (e) 10  $\Omega$
- (f) 32  $\Omega$
- (g) 50  $\Omega$
- (h) 100  $\Omega$



## Answer the Question 7

☐ a

☐ e

☐ b

☐ f

☐ c


☐ g

☐ d

☐ h

Q8. The circuit below had switch S1 in closed state and switch S2 in open state for a very long time. At  $t = 0$ , S2 is suddenly closed while S1 remains closed throughout. Assuming capacitor to be initially uncharged, what is the current  $I_{R2}$  at  $t = 0^+$ ?

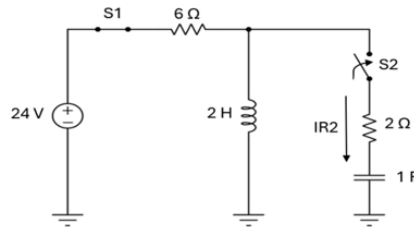- (a) -4 A
- (b) -3 A
- (c) -1 A
- (d) 0 A
- (e) 1 A
- (f) 3 A
- (g) 4 A
- (h) 12 A



## Answer the Question 8

☐ a

☐ e

☐ b

☐ f

☐ c

☐ g

☐ d

☐ h

Q9. In question 3, what is the current through  $IR_2$  at  $t = 0^+$  if the capacitor is initially charged to +4V before switch  $S_2$  is closed?


- (a) -3.5 A
- (b) -2 A
- (c) -0.5 A
- (d) 0 A
- (e) 0.5 A
- (f) 1.5 A
- (g) 3 A
- (h) 5 A

Answer the Question 9

- |                         |                         |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |
| <input type="radio"/> c | <input type="radio"/> g |
| <input type="radio"/> d | <input type="radio"/> h |

Question 10->  $I_S = 2r(t)$ . Voltage at node A at  $t = 5s$  is:

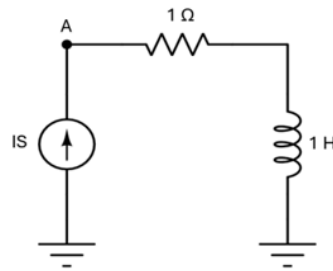- (a) -5 V
- (b) -3.2 V
- (c) -0.5 V
- (d) 0 V
- (e) 3 V
- (f) 8 V
- (g) 10 V
- (h) 12 V



Answer the Question 10

- |                         |                         |
|-------------------------|-------------------------|
| <input type="radio"/> a | <input type="radio"/> e |
| <input type="radio"/> b | <input type="radio"/> f |
| <input type="radio"/> c | <input type="radio"/> g |
| <input type="radio"/> d | <input type="radio"/> h |

Done

Powered by



Create surveys and forms with ease. [Sign up free.](#)

[Privacy & Cookie Notice](#)