2.1 Buck Converter

17/03/25 9:06 PM

Buck: ↓V by ↑I

CLOSE

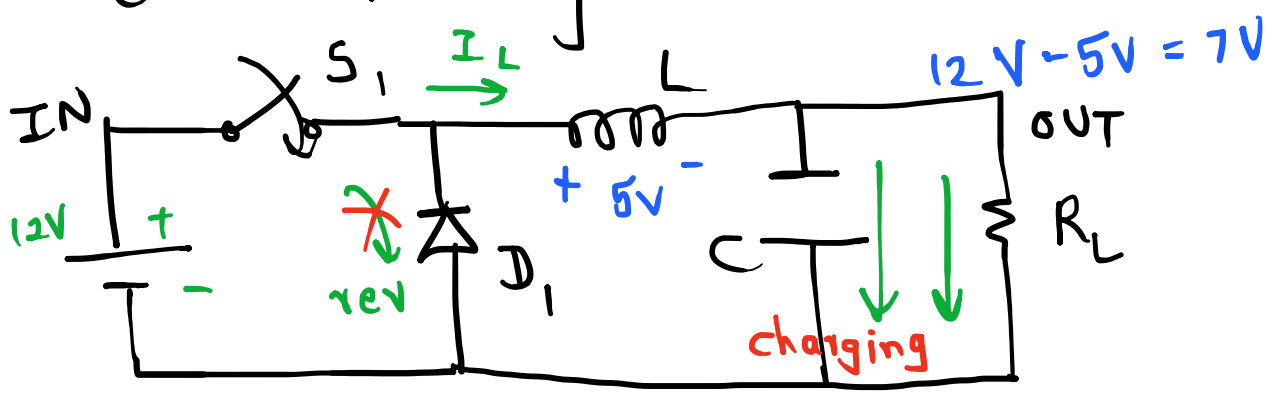

as I_L↑, B↑, E is stored in the inductor & there's a ΔV

When switch is closed: $\underbrace{V_L}_{\text{Across inductor}} = V_{out} - V_{IN}$